

# **Tutorial**

## **CSE-211**

**Q1- Indicate which of the following logic gates can be used to realize all possible combinational Logic functions**

- (a) OR gates only
- (b) NAND gates only
- (c) NOR gates only
- (d) both b and c

**Answer**

- OPTION- D
- NAND and NOR gates can be used to realize all possible combinational logic functions. That is why they are also called Universal gates.

Q2- The output of a logic gate is '1' when all its input are at logic 0. The gate is either

- (a) NAND or an EX OR gate
- (b) NOR or an EX-NOR gate
- (c) an OR or an EX NOR gate
- (d) an AND or an EX-OR gate

**Answer — -OPTION- (b)**

**If we see first gate of the given options then options (c) and (d) are ruled out as OR and AND gates give 0 output for zero inputs. Now see option (a) where NAND gate satisfies the condition but EX-OR gates does not as it gives 0 output for the same inputs. Option (b) is the correct choice where both gates satisfy the given condition.**

Q3—The Boolean function  $Y = AB + CD$  is to be realized using only 2 input NAND gates .The minimum number of gates required is

- (a) 2
- (b) 3
- (c) 4
- (d) 5


**Ans. (b)**

$$Y = AB + CD$$

**We double complement either side**


$$\begin{aligned} \text{i.e. } \overline{\overline{Y}} &= \overline{\overline{AB + CD}} \\ &= \overline{\overline{AB} \cdot \overline{CD}} \end{aligned}$$

**Logic diagram for the expression is**

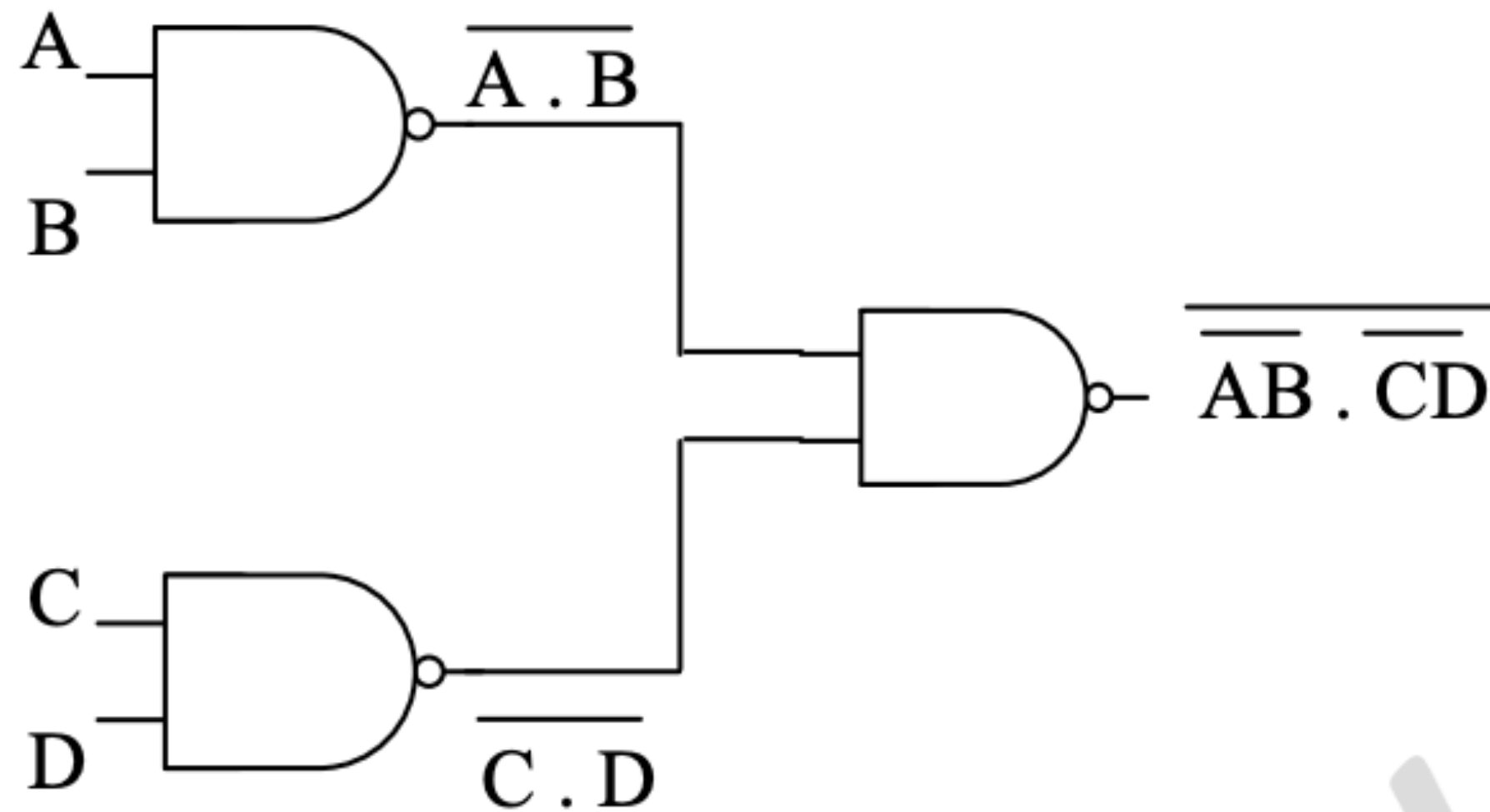

**So, requires three NAND gates**

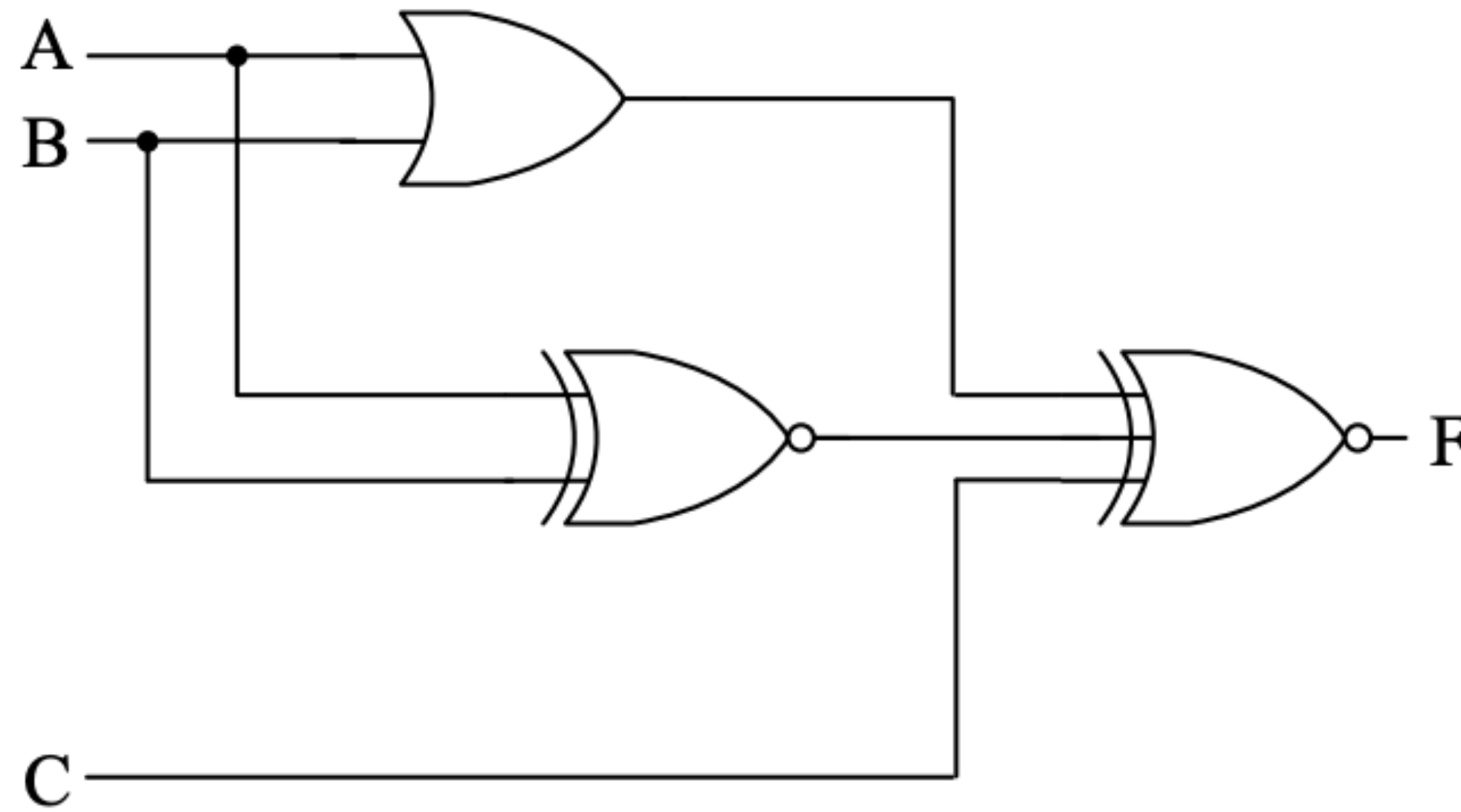**Q4.** For the output  $F$  to be 1 is the logic circuit shown, the input combination should be



- (a)  $A = 1, B = 1, C = 1$
- (b)  $A = 1, B = 0, C = 0$


- (c)  $A = 0, B = 1, C = 0$
- (d)  $A = 0, B = 0, C = 1$

**[GATE 2010: 1 Mark]**

ANSWER-4--- (d)

The same inputs A and B are connected to EX-OR and EX-NOR gates. So the Output of them will be complement of each other i.e. 0,1 or 1,0 . For F to be 1, the inputs to EX-NOR should be even (even number of 1's). For the input 1's to be even numbers C has to be 1. There is only one option with C=1 i.e. option (d).

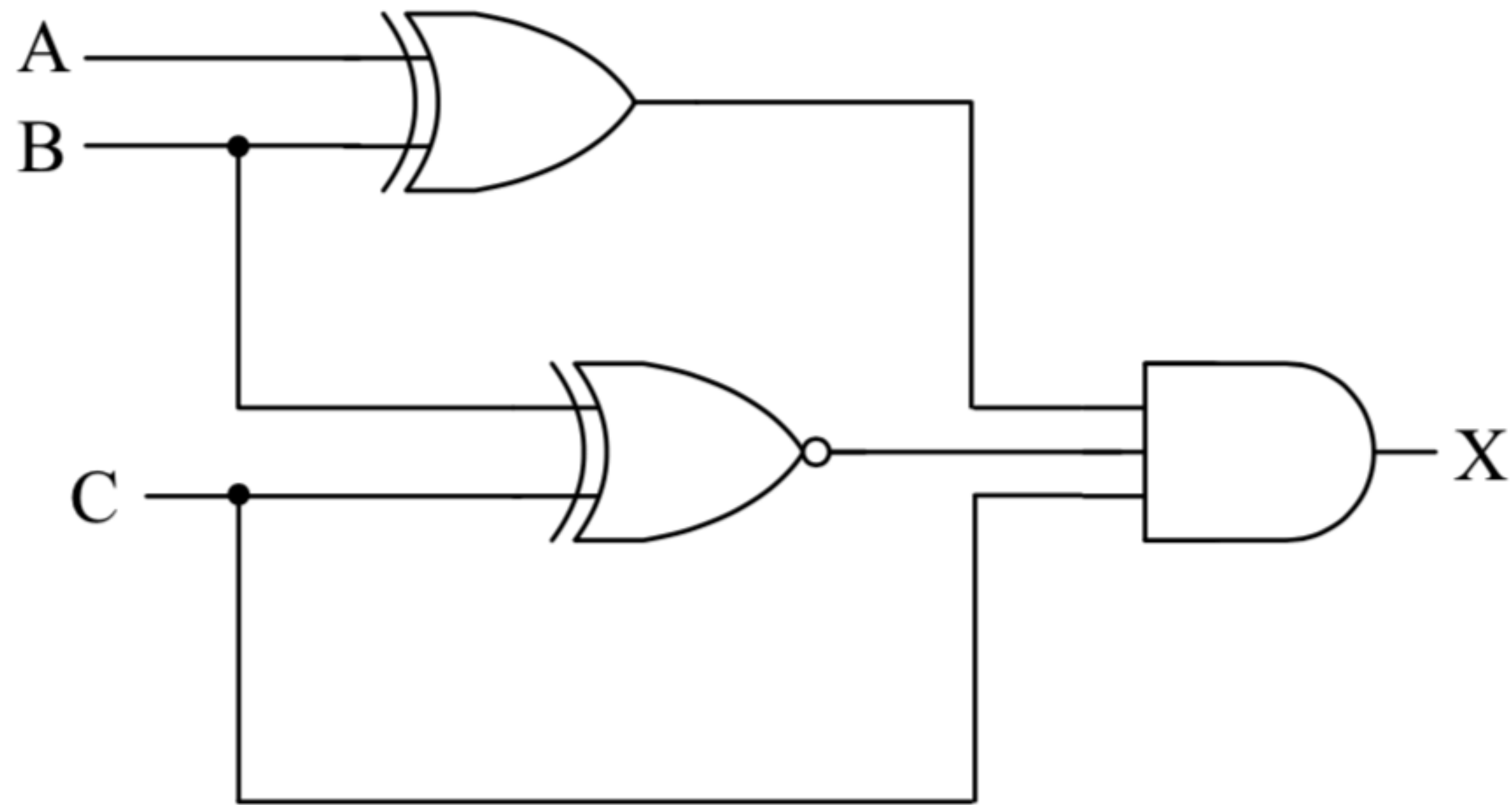**Q-5** For the logic circuit shown in the figure, the required input condition (A,B,C) to make the output  $X = 1$  is



(a) 1, 0, 1

(b) 0, 0, 1

(c) 1, 1, 1

(d) 0, 1, 1



ANSWER-5 — — —

As per the result the output  $X$  has to be 1, so all the inputs of AND gate should be 1.

i.e.  $C$  must be equal to 1.

One input to EX-NOR is 1(i.e.  $C$ )


The other input should also be 1 to get the 1 output i.e.  $B=1$

One of the input to EX-OR is 1( $B=1$ ) the other input has to be 0 to get 1 output at EX-OR Gate.

So,  $A=0$  ,  $B=1$  And  $C=1$


RIGHT Option (d)

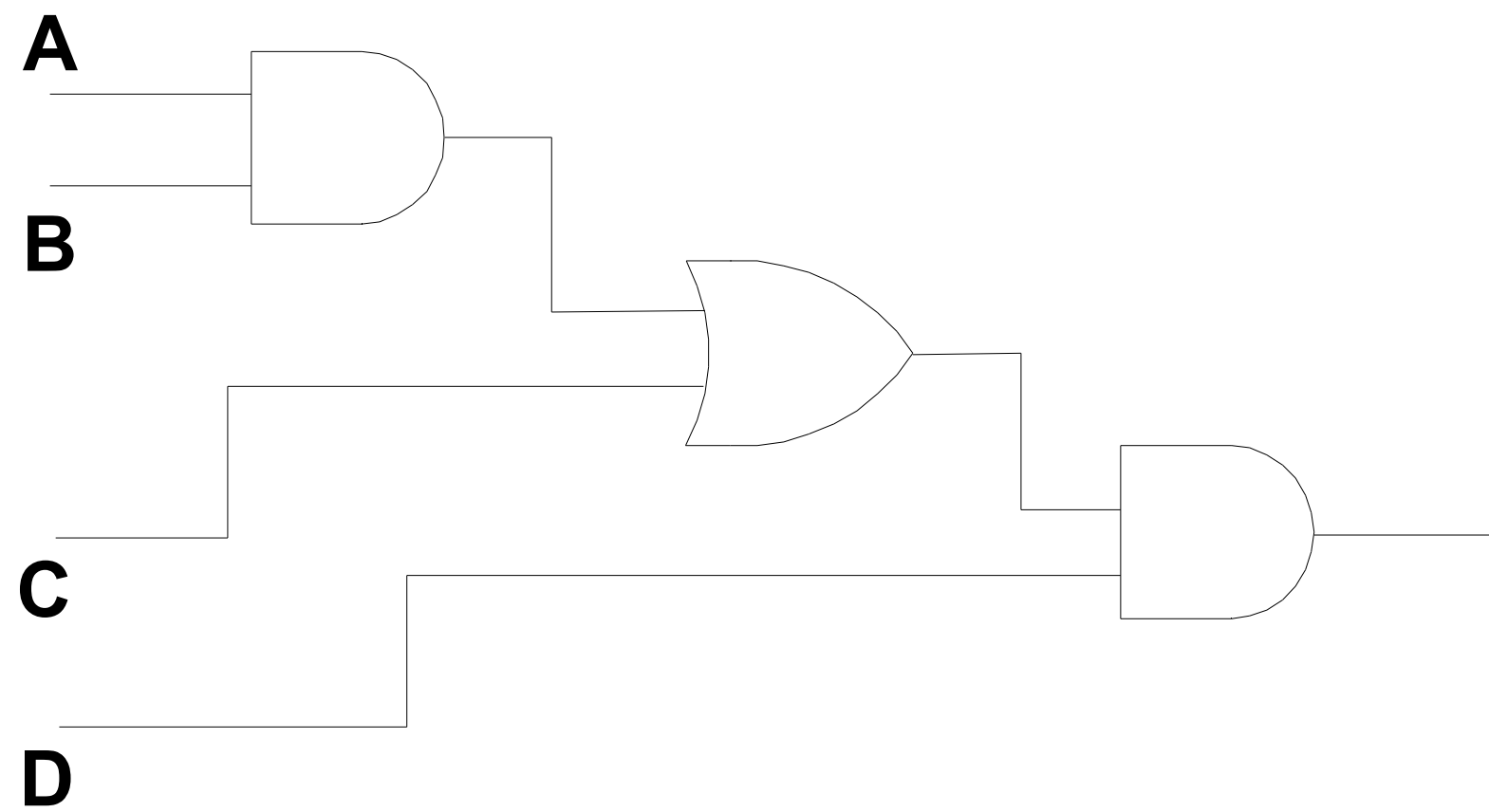Q-6- Draw a circuit diagram corresponding to the following Boolean expression:  
 $(AB + C)D$



• Q-7-

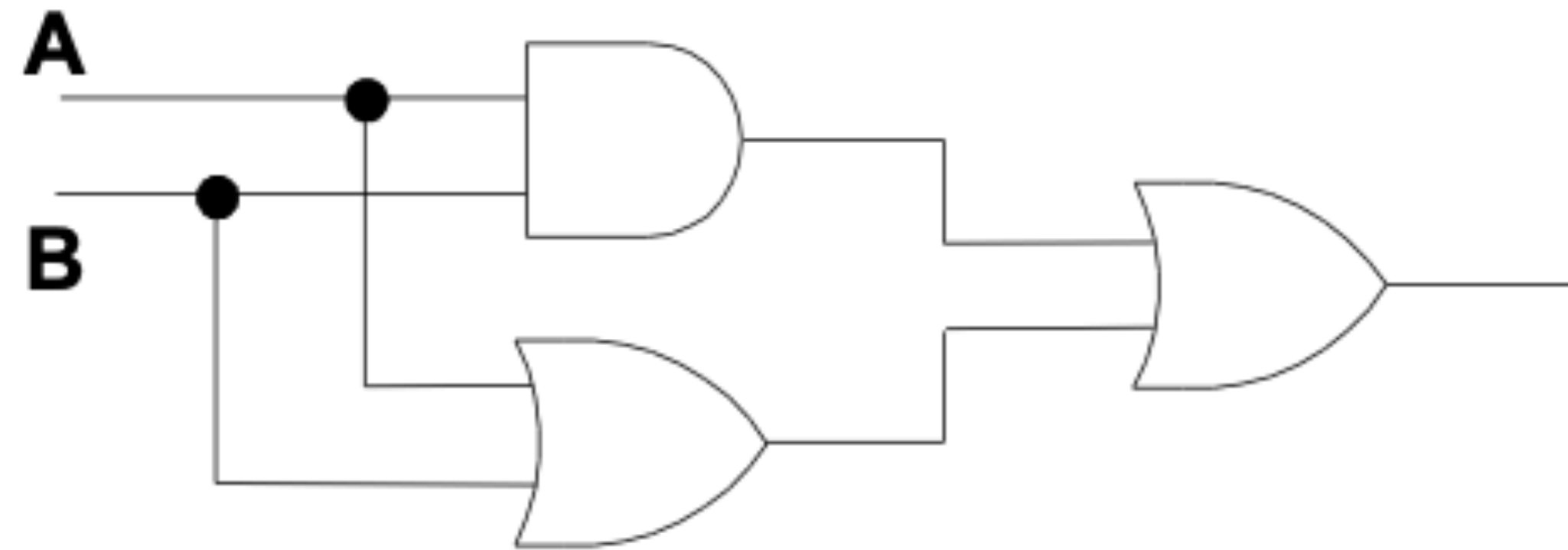Show the behavior of the following circuit with a truth table:



<b>A</b>	<b>B</b>	<b>AB</b>	<b>A+B</b>	<b>AB+(A+B)</b>
0	0	0	0	0
0	1	0	1	1
1	0	0	1	1
1	1	1	1	1

Q-8-

Electronic circuits that operate on one or more input signals to produce standard output \_\_\_\_\_

- a) Series circuits
- b) Parallel Circuits
- c) Logic Signals
- d) Logic Gates

ANSWER-8- OPTION- d


Explanation: The logic gates operate on one or more input signals to produce a standard output.

Logic gates give the output in the form of 0 and 1.

The Boolean algebra can be applied to the logic gates.

- Q-9

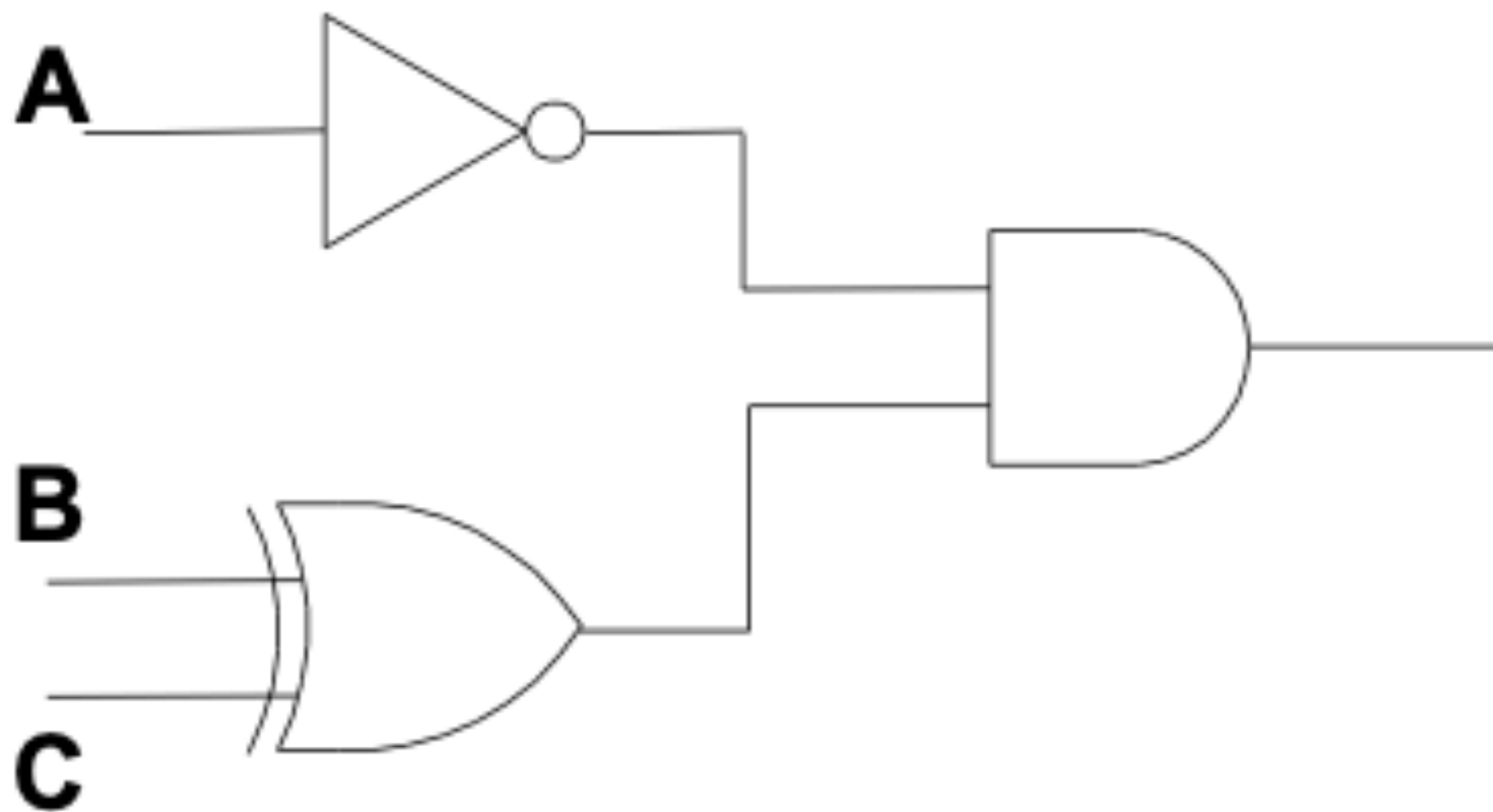Show the behavior of the following circuit with a truth table:



<b>A</b>	<b>B</b>	<b>C</b>	<b>A'</b>	<b>B⊕C</b>	<b>A'(B⊕C)</b>
0	0	0	1	0	0
0	0	1	1	1	1
0	1	0	1	1	1
0	1	1	1	0	0
1	0	0	0	0	0
1	0	1	0	1	0
1	1	0	0	1	0
1	1	1	0	0	0

C

Q-10-

The gate which is used to reverse the output obtained is \_\_\_\_\_

- a) NOR
- b) NAND
- c) EXOR
- d) NOT

Answer: d

Explanation: NOT gate is used to reverse the output from 0 to 1 and vice-versa.

The Boolean expression for NOT gate is  $Y=A'$ .

Therefore, it gives the complement of the result obtained.



