 


TUTORIAL-2


Q-1- Which of the following logic gate is represented by the following logic circuit ?

- A-NAND
- B-NOR
- C-XOR
- D-XNOR



**Q-2- CONSTRUCT 16:1 MUX
USING 4:1 MUX ONLY.**

Inputs

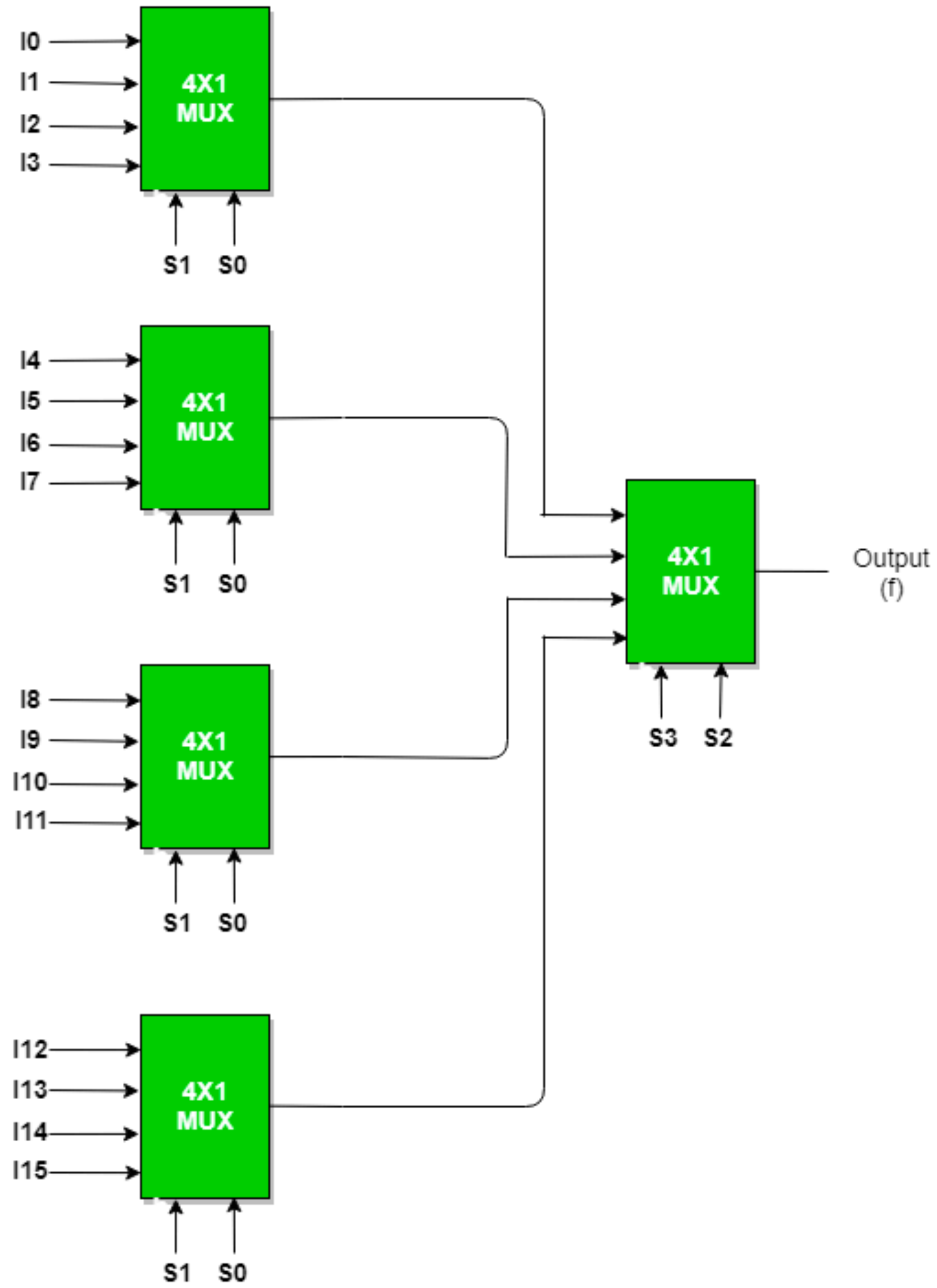

How many 3-to-8 line decoders with an enable input are needed to construct a 6-to-64 line decoder without using any other logic gates?

(A) 7


(B) 8

(C) 9

(D) 10

Answer: (C)

Explanation:

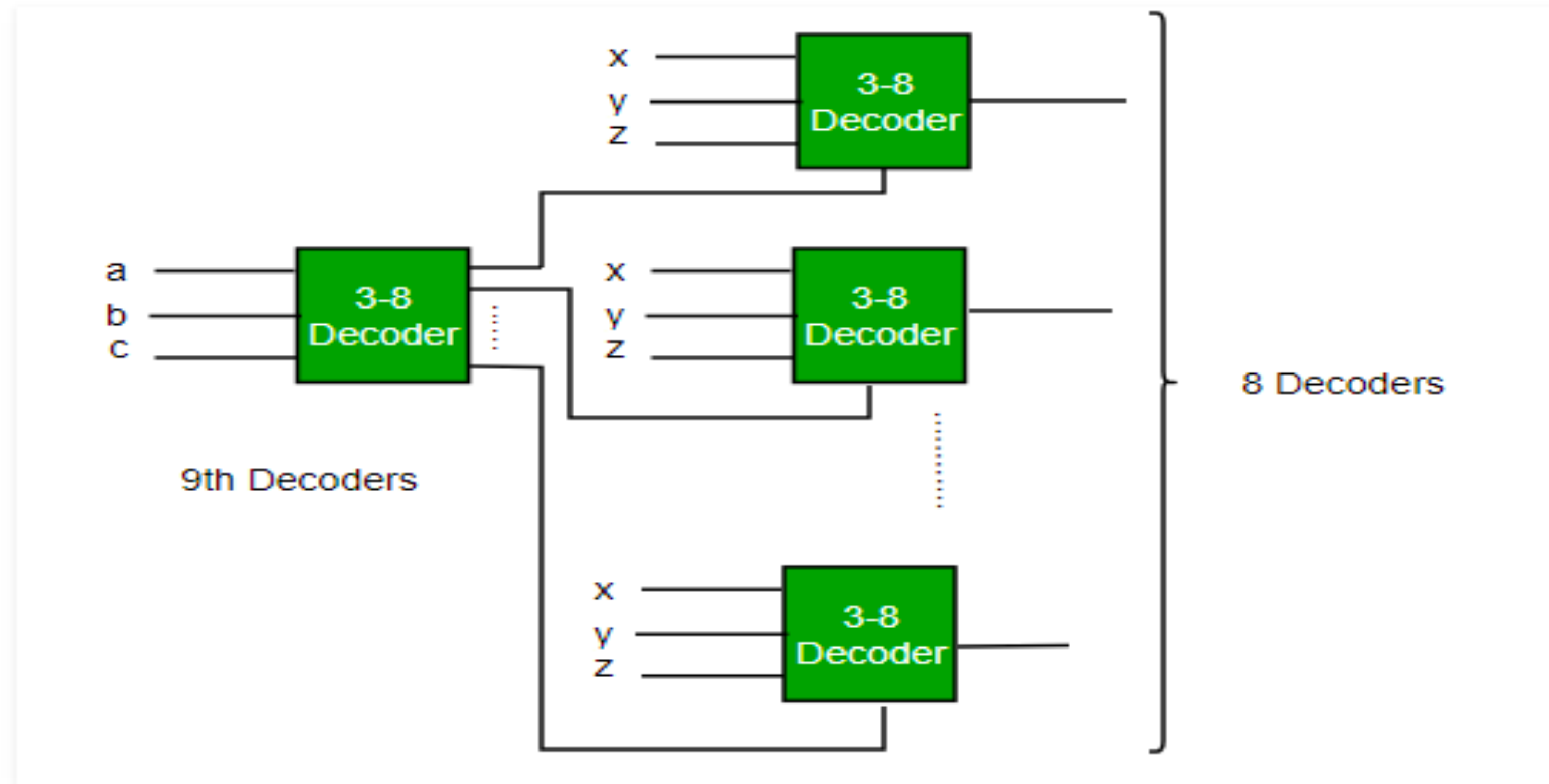


So total signals in= a, b, c, x, y, z i.e. 6

And total output = $8*8=64$

hence required decoders (from fig.) = 9 so ans is (C) part.


**Q- CONSTRUCT DECODER WITH
SIZE 3:8 USING TWO 2:4 DECODERS**

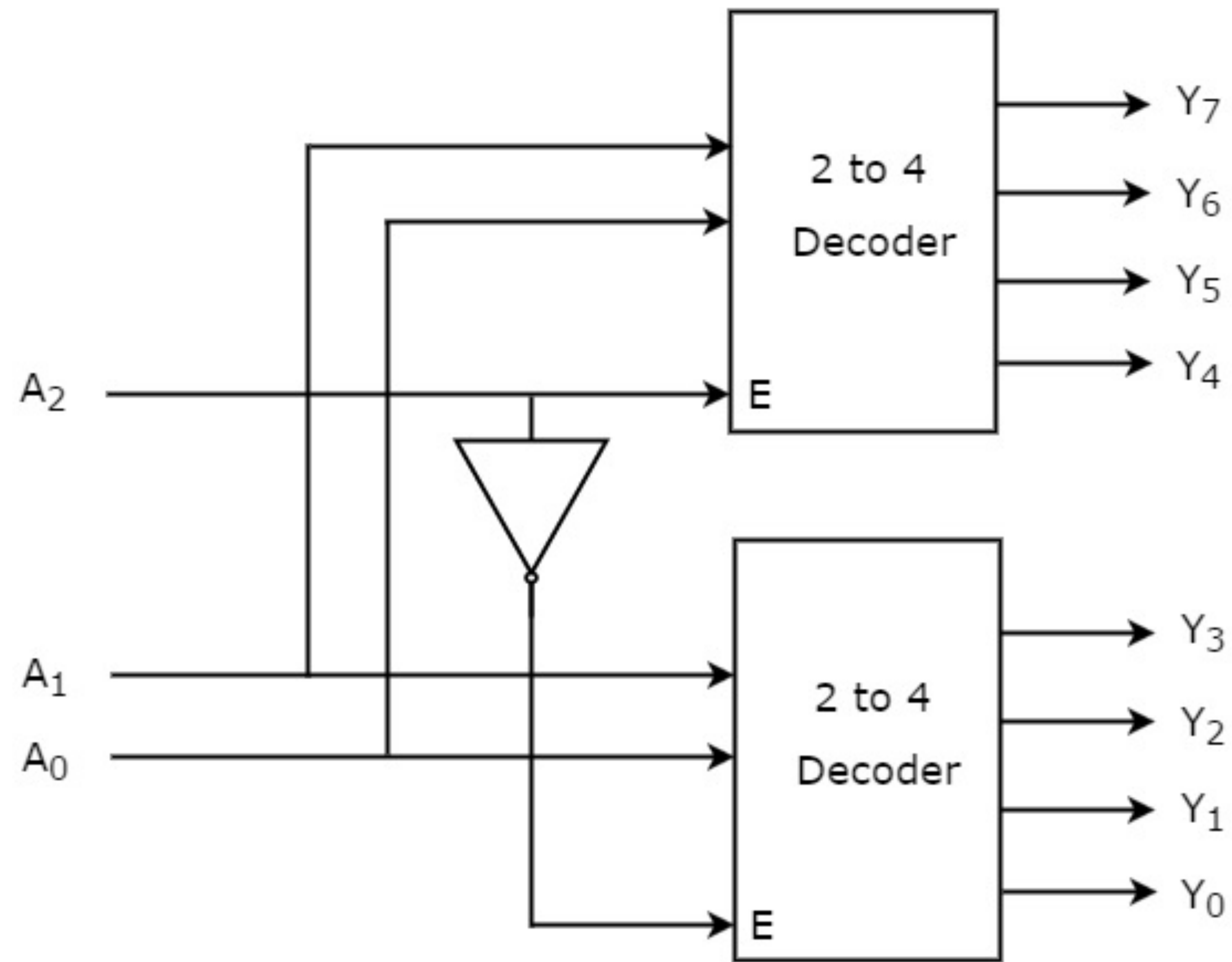Therefore, we require two 2 to 4 decoders for implementing one 3 to 8 decoder. The **block diagram** of 3 to 8 decoder using 2 to 4 decoders is shown in the following figure.



**Q- CONSTRUCT DECODER WITH
SIZE 4:16 USING TWO 3:8 DECODERS**

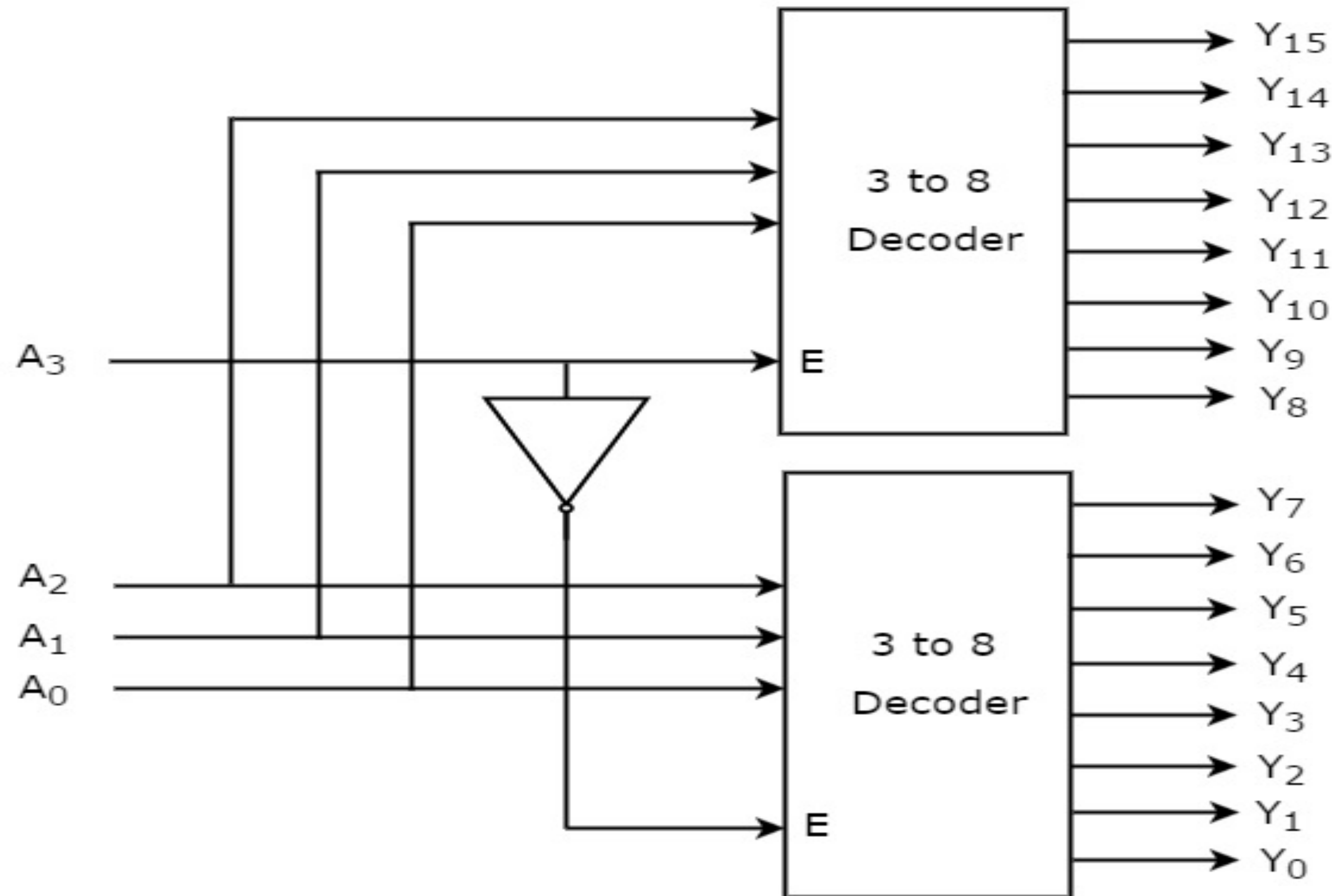Therefore, we require two 3 to 8 decoders for implementing one 4 to 16 decoder. The **block diagram** of 4 to 16 decoder using 3 to 8 decoders is shown in the following figure.



Connecting Registers - Bus Transfer

- For a bus system to multiplex **k registers** of **n bits** each
 - No. of multiplexer = n = No. of bits
 - Size of each multiplexer = k x 1, k data lines in each MUX

- **Construction of bus system for 8 register with 16 bits**
 - **16 bit register X 8**
 - **16 MUX 8X1 multiplexer— NO OF MUX REQUIRED**
 - **Bus selection S0, S1, S2**

